



KING FAISAL UNIVERSITY
COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRICAL ENGINEERING



Course Code / Title: **BME 310 –Bio-Electronics I**

Semester / Year: **Fall /2019**

Homework Assignment #: **3**


Date: **23/10/2019**

Due Date: **3/11/2019**

Instructor: **Dr. Mohammed Morsy Farag**

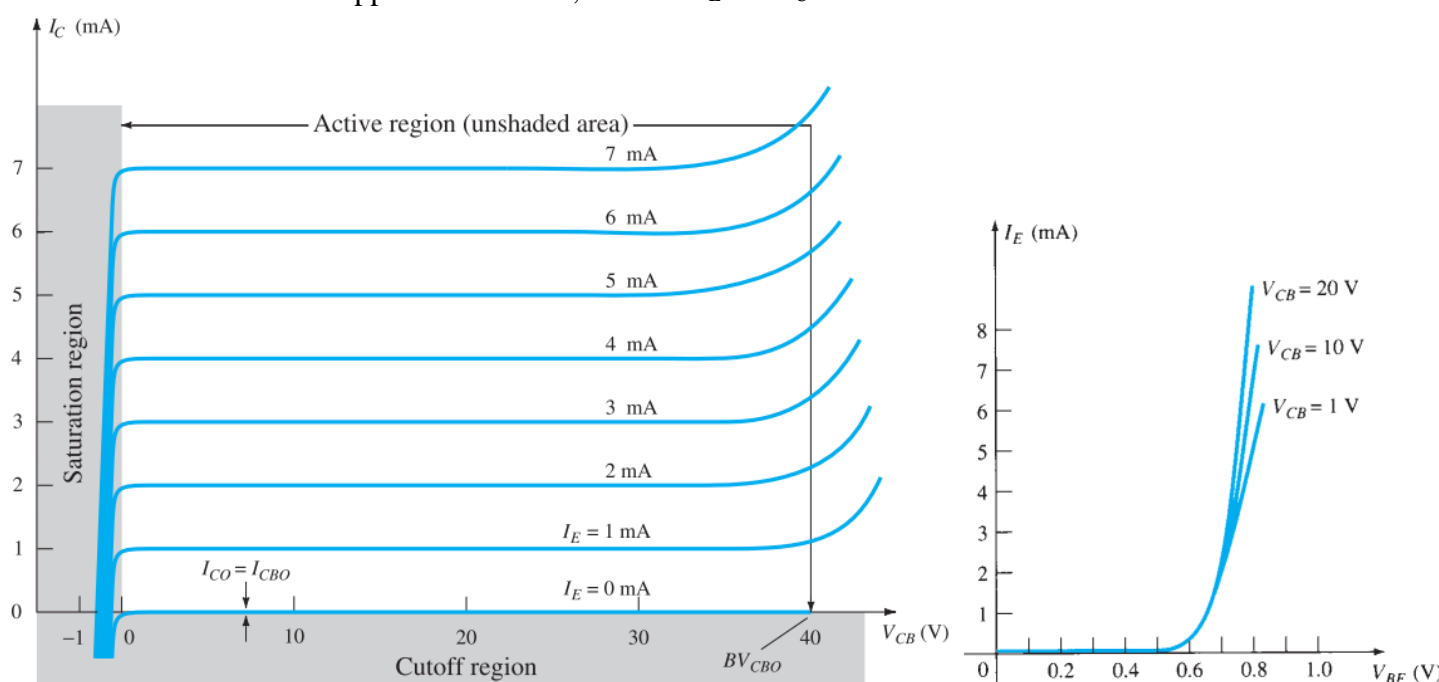1. Find the following for a transistor in the Common-Base Configuration

- Using the characteristics of Fig. P1, determine the resulting collector current if $I_E = 3.5$ mA and $V_{CB} = 10$ V.
- Repeat part (a) for $I_E = 3.5$ mA and $V_{CB} = 20$ V.
- How have the changes in V_{CB} affected the resulting level of I_C ?
- On an approximate basis, how are I_E and I_C related based on the results above?



2.



- Using the characteristics of Fig. P1, determine I_C if $V_{CB} = 5$ V and $V_{BE} = 0.7$ V.
- Determine V_{BE} if $I_C = 5$ mA and $V_{CB} = 15$ V.

3. Find the following for a transistor in the Common-Base Configuration

- Given α_{dc} of 0.998, determine I_C if $I_E = 4$ mA.
- Determine α_{dc} if $I_E = 2.8$ mA, $I_C = 2.75$ mA and $I_{CBO} = 0.1$ μ A.

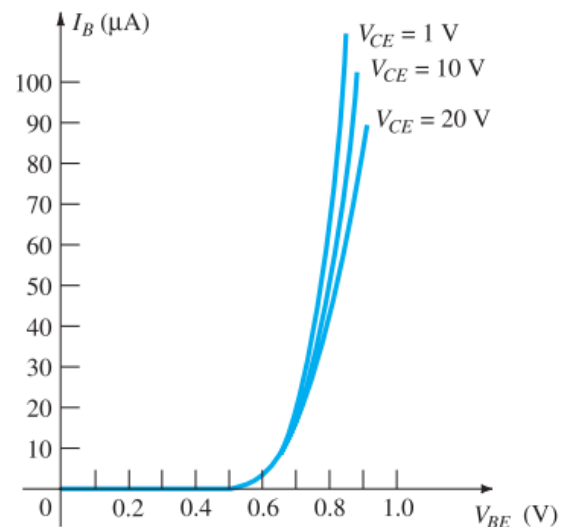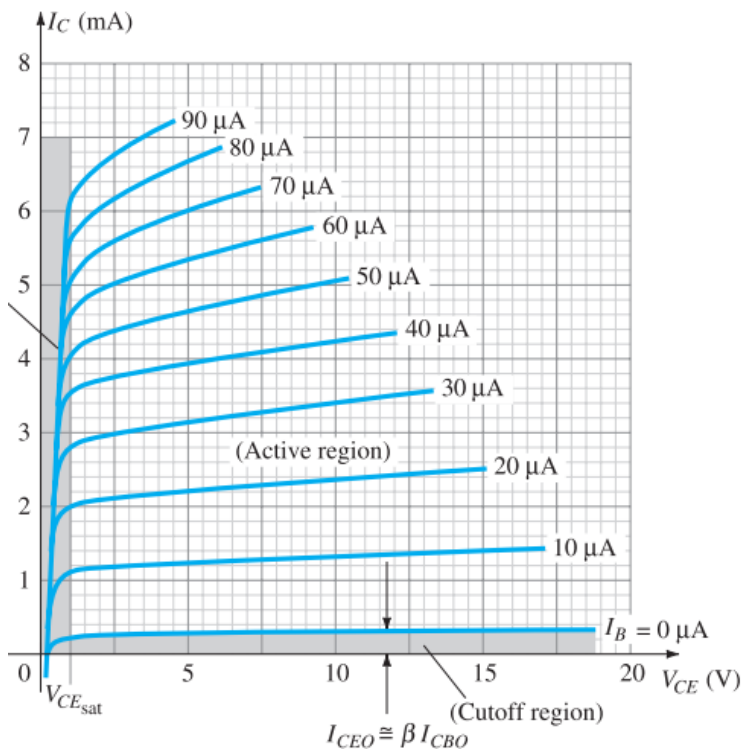4. Using the characteristics of Figure P4 for a transistor in the Common-Emitter Configuration:

- Find the value of I_C corresponding to $V_{BE} = +750$ mV and $V_{CE} = +4$ V.
- Find the value of V_{CE} and V_{BE} corresponding to $I_C = 3.5$ mA and $I_B = 30$ μ A.



5. For the common-emitter characteristics of Fig. P4
 - a. Find β_{dc} at an operating point of $V_{CE} = 6 V$ and $I_C = 2 mA$.
 - b. Find the value of α corresponding to this operating point.
 - c. At $V_{CE} = +6 V$, find the corresponding value of I_{CEO} .
 - d. Calculate the approximate value of I_{CBO} using β_{dc} value obtained in part (a).
6. Using the characteristics of Fig. P4:
 - a. Determine I_{CEO} at $V_{CE} = 10 V$.
 - b. Determine β_{dc} at $I_B = 10 \mu A$ and $V_{CE} = 10 V$.
 - c. Using β_{dc} determined in part (b), calculate I_{CBO} .
7. Using the characteristics of Fig. P4, determine β_{dc} at $I_B = 25 \mu A$ and $V_{CE} = 10 V$. Then calculate α_{dc} and the resulting level of I_E .
8. For a BJT in the common-emitter configuration:
 - a. Given that $\alpha_{dc} = 0.980$, determine the corresponding value of β_{dc} .
 - b. Given $\beta_{dc} = 120$, determine the corresponding value of α .
 - c. Given that $\beta_{dc} = 120$ and $I_C = 2.0 mA$, find I_E and I_B .
9. An input voltage of $2 V$ rms (measured from base to ground) is applied to the circuit of Fig. P9. Assuming that the emitter voltage follows the base voltage exactly and that $V_{be}(rms) = 0.1 V$, calculate the circuit voltage amplification ($A_v = V_o/V_i$) and emitter current for $R_E = 1 k\Omega$.

